

T.C. Trakya University
Faculty of Engineering
Department of Electrical and Electronics Engineering
Assist. Prof. Işık İlber Sırmatel

EEM/EEE314 Automatic Control Systems

Exam-style questions with solutions

Part 3: Electromechanical systems


Abbreviations:

emf: electromotive force


KVL: Kirchhoff's voltage law

N2L: Newton's second law of motion

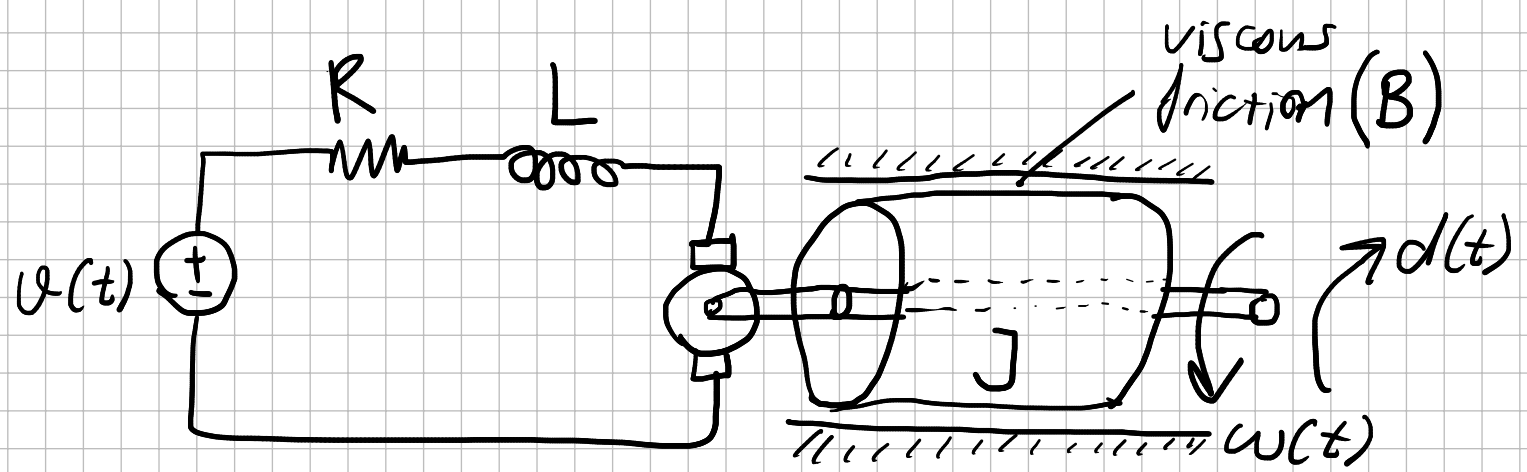Question 1: Consider the schematic of an rotational electromechanical system (DC motor) depicted below, consisting of a resistor and an inductor (with parameters R and L) for the electrical part, and a rotating object with a moment of inertia of J and a viscous friction element with constant B , for the mechanical part. The motor torque constant K_m is equal to the back electromotive force constant K_b , and is given as K (that is, $K = K_m = K_b$). Angular velocity of the mass is denoted as $\omega(t)$. An external voltage is being applied to the system, denoted as $v(t)$. An external load torque is being applied to the system, denoted as $d(t)$. There are no other forces or torques acting on the system. Find the differential equation model of the system relating $v(t)$, $d(t)$ and $\omega(t)$.



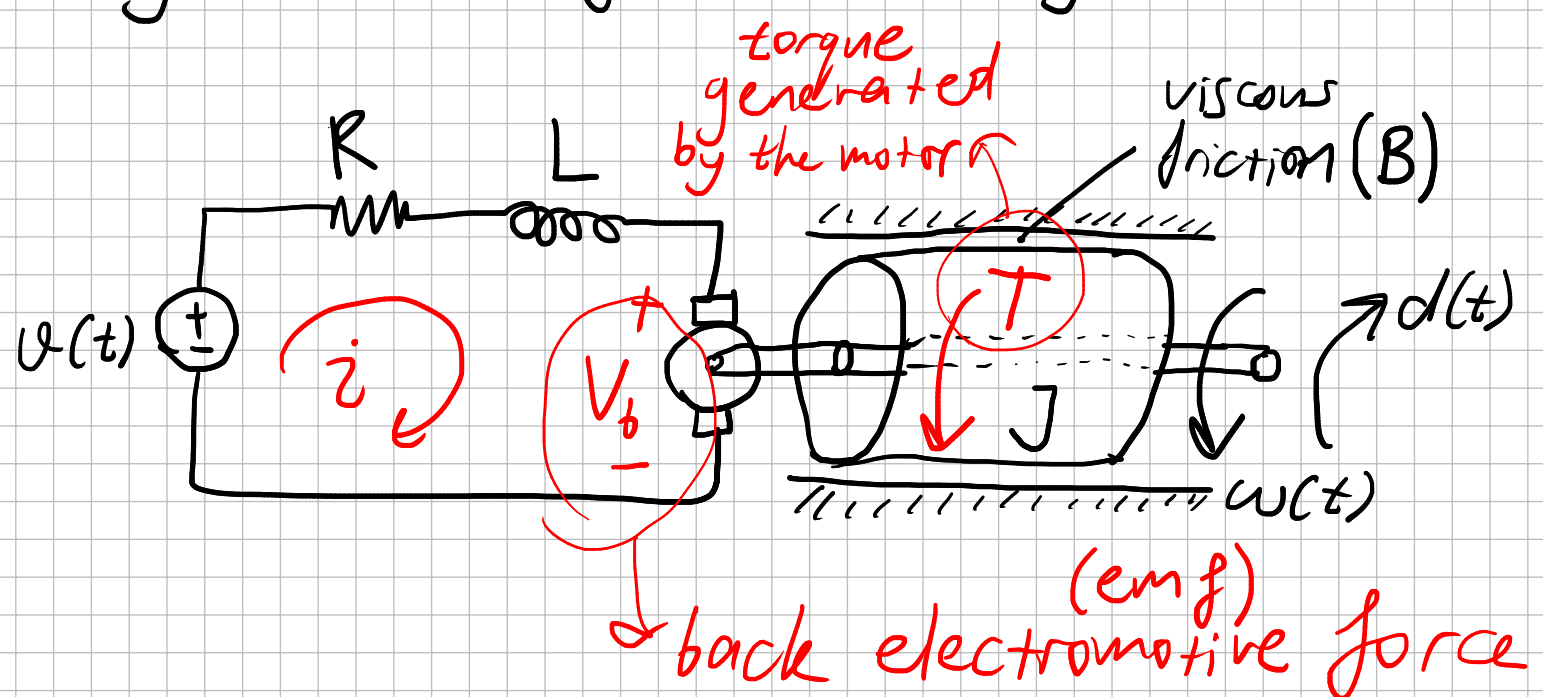Solution: Define the following symbols for the system:



Note that T and ω have the same direction, while d is in the opposite direction.

↳ We should notice this from the system schematic given in the question.

Writing KVL for the electrical part:

$$V = V_R + V_L + V_b$$

From linear models of R and L elements:

$$V_R = R \cdot i \quad V_L = L \cdot \dot{i}$$

Thus, KVL becomes:

$$V = R \cdot i + L \cdot \dot{i} + V_b$$

Writing NZL for the rotational motion of the mechanical part:

$$\sum_i T = J \cdot \dot{\omega}$$

$$T - d - B \cdot \omega = J \cdot \dot{\omega}$$

torque
generated
by the
motor

external
load
torque

torque due
to viscous
friction

The torque-current relationship is as follows: $T = K \cdot i$

The back emf-speed relationship is as follows: $V_b = K \cdot \omega$

Substituting these into KVL and NZL:

$$V = R \cdot i + L \cdot \dot{i} + K \cdot \omega$$

$$J \dot{\omega} + B \omega - K \cdot i = -d$$

Rewriting this for i alone:

$$i = \frac{J \dot{\omega} + B \omega + d}{K}$$

Differentiating both sides:

$$\dot{i} = \frac{J \ddot{\omega} + B \dot{\omega} + \dot{d}}{K}$$

Substituting these in KVL:

$$\begin{aligned} \varrho = & \frac{RJ}{K} \dot{\omega} + \frac{RB}{K} \omega + \frac{R}{K} d + \dots \\ & + \frac{LJ}{K} \ddot{\omega} + \frac{LB}{K} \dot{\omega} + \frac{L}{K} \dot{d} + K\omega \end{aligned}$$

Simplifying by gathering ω and $\dot{\omega}$ terms together:

$$\frac{LJ}{K} \ddot{\omega} + \frac{RJ+LB}{K} \dot{\omega} + \left(\frac{RB}{K} + K \right) \omega = \dots$$

$$\dots \varrho - \frac{L}{K} \dot{d} - \frac{R}{K} d$$